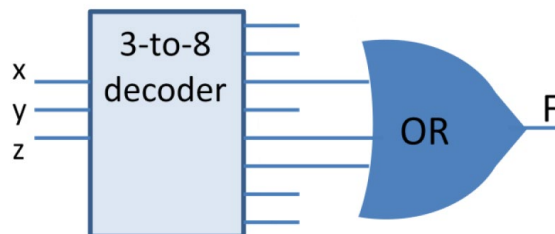



# CDA 3103 Computer Organization Homework
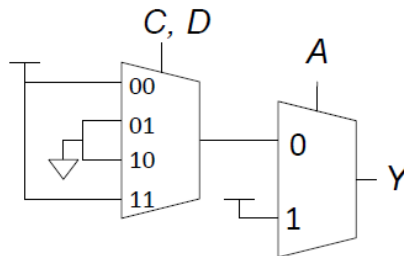
## Section I: Problems


- (15 points) Assume the output of the decoder in the following picture is ordered as 0 to 7 from top to bottom. Write the Boolean function implemented in Canonical Sum-of-Product format and Canonical Product-of-sum format.




- (10 points) Write a simplified Boolean function for the function performed by the circuit below.



- (20 points) A seven-segment display decoder takes a 4-bit data input  $D_{3:0}$  and produces seven outputs to control light-emitting diodes to display a digit from 0 to 9. The seven outputs are often called segments a through g, or  $S_a$ - $S_g$ , as defined in the following figure (a). The digits are shown in figure (b). Write a true table for the outputs, then use Boolean identities to find the simplified Boolean functions for outputs  $S_a$  and  $S_b$ . Assume that illegal input values (10-15) produce a blank readout.

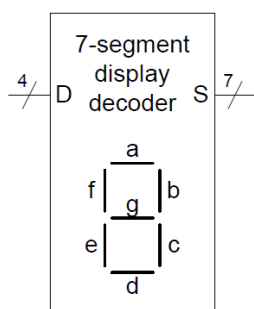


(a) Seven-segment display decoder icon

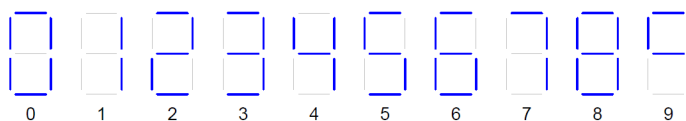


(b) Seven-segment display digits

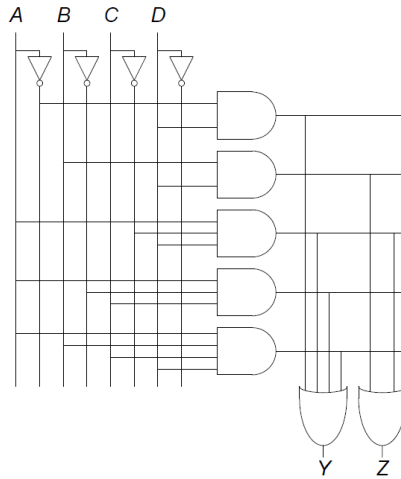4. (10 points) Using a 4X16 decoder module and a OR gate to implement the Boolean function  $f(a, b, c, d) = abc' + acd$ .
5. (10 points) Using an 8X1 multiplexer module to implement the Boolean function  $f(a, b, c) = b + ac'$ .
6. (10 points) Write Boolean functions for the circuit below in Canonical sum-of-product form.



7. (10 points) Simplify the Boolean functions from problem 6 and sketch an improved circuit with the same function.
8. (15 points) Complete the truth table for the following sequential circuit:

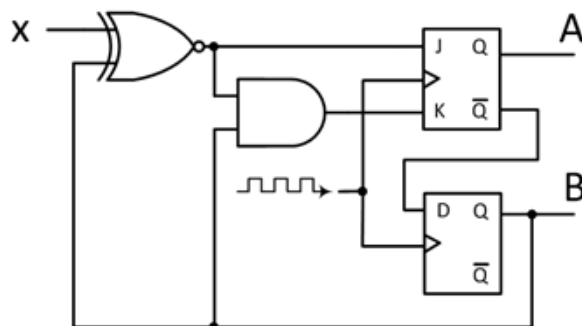[illegible]

## **Section II: Submission Requirements**

The following requirements are for electronic submission via Canvas.

- Your solutions must be in a single file with a file name yourname-module3-assignment-2.
- Upload the file by following the link where you download the homework description on Canvas.
- If scanned from hand-written copies, then the writing must be legible, or loss of credits may occur.
- Only submissions via the link on Canvas where this description is downloaded are graded. Submissions to any other locations on Canvas will be ignored.