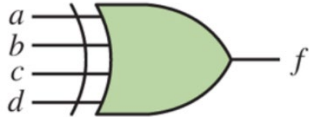


CDA 3103 Computer Organization Homework


Section I: Problems

1. (10 points) Construct true tables for the following XOR and XNOR gates.

(a)



(b)

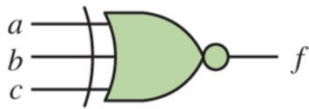

2. (10 Points) Write the Boolean expression in Canonical sum-of-products and Canonical product-of-sum forms for the following truth table.

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

3. (10 points) Use Boolean Identities to simplify the Canonical sum-of-product Boolean function obtained in problem 2.
4. (10 Points) Write the Boolean expression in Canonical sum-of-products and Canonical product-of-sum forms for the following truth table.

w	x	y	z	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0

0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

5. (10 points) Use Boolean Identities to simplify the Canonical sum-of-product Boolean function obtained in problem 4.
6. (10 points) find CSOP and CPOS forms for the following functions:
 - a) $F(a, b, c) = ab + a'c$
 - b) $F(A, B, C, D) = A(B' + CD') + A'BC'D$
7. (40 Points) Use Boolean Identities to simplify the following Boolean functions:
 - a) $xyz' + xy'z' + x'yz + x'y'z' + xyz$
 - b) $wxy'z + wxyz' + wxy'z' + wx'y'z + wx'y'z' + w'xy'z + w'x'y'z + w'x'y'z'$
 - c) $w'x'y' + w'xz + wxz + wx'y'z'$
 - d) $(X + Y + Z + W')(V + X)(V' + Y + Z + W')$

Section II: Submission Requirements

The following requirements are for electronic submission via Canvas.

- Your solutions must be in a single file with a file name yourname-module3-assignment-1.
- Upload the file by following the link where you download the homework description on Canvas.
- If scanned from hand-written copies, then the writing must be legible, or loss of credits may occur.
- Only submissions via the link on Canvas where this description is downloaded are graded. Submissions to any other locations on Canvas will be ignored.